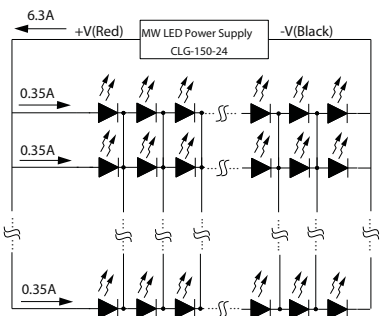
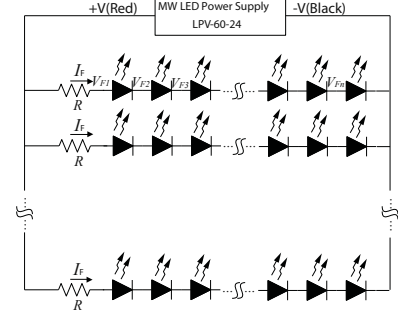
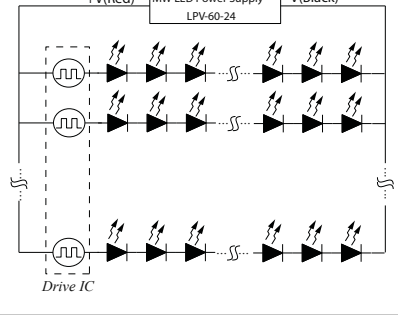


HOW TO CHOOSE A SUITABLE LED POWER SUPPLY?

- Decide a suitable wattage level, including safety margin.
- Verify your design of LED driving circuit: direct drive by PSU [choose a constant current (C.C.) mode LED power supply] or add additional driving IC to get a more precise constant current level [choose a constant voltage (C.V.) or constant current (C.C.) mode LED power supply].
- Verify whether the application need PFC function.
- Verify location of assembly and the required level against dust and humidity for the LED power supply (enclosure style and IP level).
- Verify the required safety certificates.
- Need to adjust the output voltage and/or output current or need the dimming function ?

■ Suggested System Design

Setting	Circuit diagram	Description	Advantage & Disadvantage
<p>Use C.C. mode power supply</p> <p>No need ballast resistor and LED driver IC</p>	 <p>For 1W LED, $V_F=3.2V$, $I_F=0.35A$ Parallel connection: $6.3A / 0.35A=18$ 18 branches need to connect in parallel</p> <p>Constant current region of CLG-150-24: $12\sim 24V$, so the LED series connection should be 4 to 7.</p>	<p>Using Mean Well power supply as the constant current source and feed the LED arrays directly.</p>	<p>Advantage: The cost and complexity are the lowest to LED manufacturers. Just need to consider about characteristics of the LED.</p> <p>Disadvantage: Driving current for each branch may be unbalance</p>
<p>Use C.V. or C.C. mode power supply</p> <p>Add ballast resistor to balance every branch</p>		$R = [V - (V_{F1} + V_{F2} + \dots + V_{Fn})] / I_F$ <p>Note: V: Rated output voltage of LED power supply V_F: LED's forward voltage I_F: LED's forward current</p> <p>Example: Using LPV-60-24(24V/2.5A) to drive a LED array which 6 LEDs connected in series in each branch and 4 branches connected in parallel $R = [24 - (6 \times 3)] / (2.5 / 4) = 10\Omega$</p>	<p>Advantage:</p> <ul style="list-style-type: none"> • Low cost • Simple <p>Disadvantage:</p> <ul style="list-style-type: none"> • Brightness of LED is uneven • Poor efficiency
<p>Use C.V. or C.C. mode power supply</p> <p>Driver IC is used as a constant current source (without ballast resistor)</p>		<p>PWM constant current source will regulate forward current to achieve even current at each branch</p>	<p>Advantage:</p> <ul style="list-style-type: none"> • High efficiency • Perfect current balance to each branch • Longer lifetime for LEDs <p>Disadvantage:</p> <ul style="list-style-type: none"> • Highest cost • High complexity • EMC problem at lighting equipment side